

# Digital IC Design

---

CHENCHETY ABHISHEK

EE20BTECH11012

## Assignment-1

### Question-2

- Implement  $f = x_0h_0 + x_1h_1 + x_2h_2 + x_3h_3 + x_4h_4 + x_5h_5 + x_6h_6 + x_7h_7 + x_8h_8 + x_9h_9$  keeping in mind that **no two different arithmetic operations will take place in same clock edge**.

### Verilog code

```
// Evaluating final result at every alternate posedge of clk

// Declaring module with the required in and out parameters
module
Q2(out,clk,adder_clk,x_0,x_1,x_2,x_3,x_4,x_5,x_6,x_7,x_8,x_9,h_0,h_1,h_2,h_3,h_4,h
_5,h_6,h_7,h_8,h_9);

// Given input of 4 bit
input
[3:0]x_0,x_1,x_2,x_3,x_4,x_5,x_6,x_7,x_8,x_9,h_0,h_1,h_2,h_3,h_4,h_5,h_6,h_7,h_8,h
_9;

// expected 11 bit output
output reg [10:0]out;

//Creating Registers for storing multiplied values
reg [7:0]m0,m1,m2,m3,m4,m5,m6,m7,m8,m9;

// Count var for implementation control

input clk;
input adder_clk;

always @(posedge clk ) begin
    m0<=x_0*h_0;
    m1<=x_1*h_1;
    m2<=x_2*h_2;
    m3<=x_3*h_3;
    m4<=x_4*h_4;
    m5<=x_5*h_5;
    m6<=x_6*h_6;
    m7<=x_7*h_7;
    m8<=x_8*h_8;
    m9<=x_9*h_9;

end
```

```

always @(negedge adder_clk ) begin
    out<= m0+m1+m2+m3+m4+m5+m6+m7+m8+m9;
end
endmodule

```

## Testbench code

```

`timescale 1ns/1ns
`include "Q2.v"

module Q2_tb;

// Declaring Port parameters for testbench
reg
[3:0]x_0,x_1,x_2,x_3,x_4,x_5,x_6,x_7,x_8,x_9,h_0,h_1,h_2,h_3,h_4,h_5,h_6,h_7,h_8,h_9;
reg clk=1'b1;
reg adder_clk=1'b1;
wire [10:0]Output;

// Clock pulse generation
always #1 clk = ~clk;
always #2 adder_clk = ~adder_clk;

Q2
 uut(Output,clk,adder_clk,x_0,x_1,x_2,x_3,x_4,x_5,x_6,x_7,x_8,x_9,h_0,h_1,h_2,h_3,h_4,h_5,h_6,h_7,h_8,h_9);

// Declaring variables for testbench
integer testcases,expected_out;
// Monitoring the input values & Output
initial begin
    $monitor($time,"x_0=%d x_1=%d x_2=%d x_3=%d x_4=%d x_5=%d x_6=%d x_7=%d x_8=%d
x_9=%d h_0=%d h_1=%d h_2=%d h_3=%d h_4=%d h_5=%d h_6=%d h_7=%d h_8=%d h_9=%d
Output=%d
expected=%d",x_0,x_1,x_2,x_3,x_4,x_5,x_6,x_7,x_8,x_9,h_0,h_1,h_2,h_3,h_4,h_5,h_6,h_7,h_8,h_9,Output,expected_out);

    $dumpfile("Q2.vcd");
    $dumpvars;

    #30 $finish;
end

// Running testcases
initial begin
    for (testcases=0; testcases<10; testcases++) begin
        #4
        x_0=$random;x_1=$random;x_2=$random;x_3=$random;x_4=$random;x_5=$random;x_6=$random;
x_7=$random;x_8=$random;x_9=$random;h_0=$random;h_1=$random;h_2=$random;h_3=$random;
h_4=$random;h_5=$random;h_6=$random;h_7=$random;h_8=$random;h_9=$random;


```

```


        expected_out = x_0*h_0 + x_1*h_1 + x_2*h_2 + x_3*h_3 + x_4*h_4 +
        x_5*h_5 + x_6*h_6 + x_7*h_7 + x_8*h_8 + x_9*h_9;
    end
end
endmodule

```

## Output on GTKWave

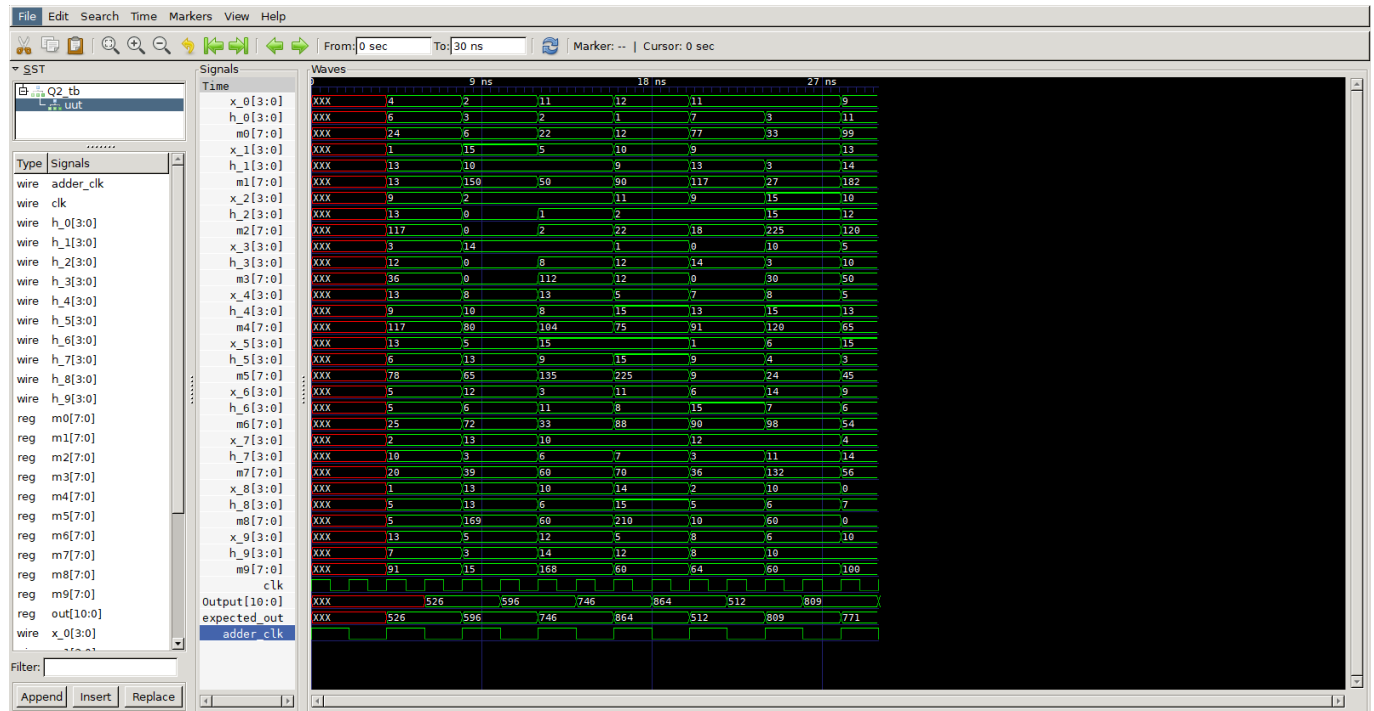

## Verification through synthesis

 

- 10 Multiplier modules and 9 adder modules are used in this case i.e same as discussed in class.